

1 Driver Amplifier

First, the Driver Amplifier was built. The associated schematic can be seen in Figure 1.

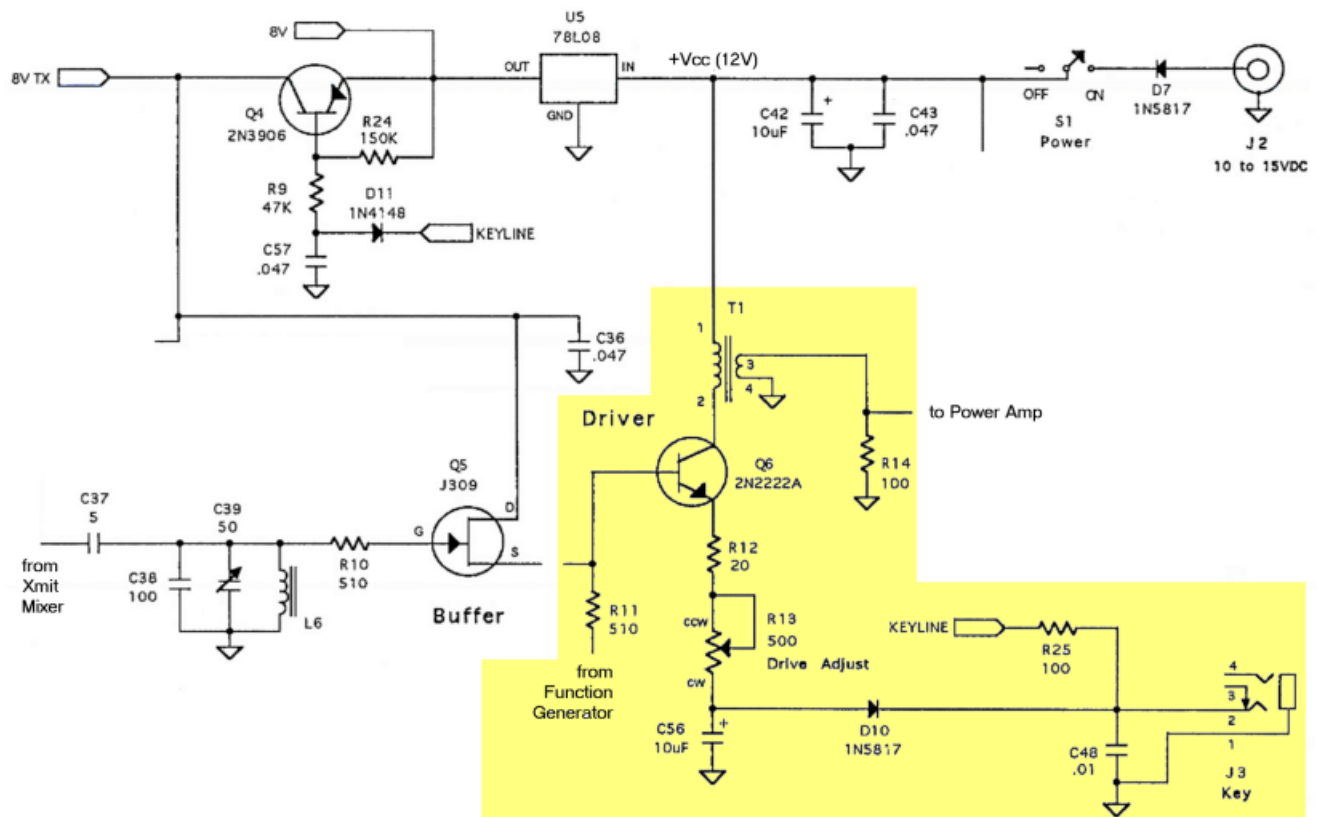


Figure 1: Circuit Schematic for the Driver Amplifier

1.1 Measured Output Voltage: V_{out}

With the function generator set to 7.04MHz, and with an offset of 0.5V. The output voltage across R_{14} was measured to be $\boxed{2.16V_{RMS}}$. The voltage observed was high, which threw off the following calculated values.

1.2 Calculated Output Power: P

P is calculated using the following:

$$P = \frac{V_{RMS}^2}{R_{14}} \Rightarrow \frac{2.16^2}{100\Omega} = \boxed{47mW}$$

1.3 Calculated Supply Power: P_0

1.3.1 $V_{R_{12}}$

The DC voltage across R_{12} , $V_{R_{12}}$ was recorded to be $\boxed{594mV}$.

1.3.2 i_E

The emitter current, i_E , was found by:

$$i_E = \frac{V_{R_{12}}}{R_{12}} \Rightarrow \frac{595mV}{20\Omega} = \boxed{29.8mA}$$

1.3.3 Supply Power: P_0

V_{cc} was measured at the small resistor across S_1 , and found to be $\boxed{9.72V}$. Therefore, the DC supply power $P_0 = (V_{cc} \cdot i_E) = \boxed{289mW}$

1.4 System Efficiency: η

The efficiency η was calculated to be:

$$\eta = \frac{P}{P_0} \Rightarrow \frac{47mW}{289mW} \approx \boxed{16\%}$$


1.5 Amplifier Gain: G

The gain G was found to be:

$$G = 10\log\left(\frac{P}{P_0}\right) \Rightarrow 10\log\left(\frac{47mW}{289mW}\right) = \boxed{-7.9dB}$$

Since the resistor R_{13} was fully clockwise, this meant that $G = G_{v(Max)}$. When R_{13} is fully counter-clockwise (min), the voltage gain was found to be:

$$G_{v(Min)} = 10\log\left(\frac{15.6\mu W}{132\mu W}\right) = \boxed{-9.3dB}$$

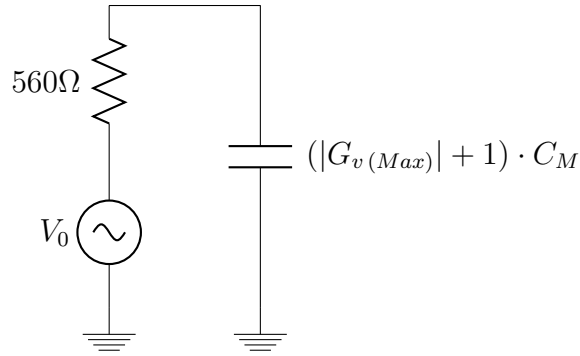Figure 2: Equivalent circuit for extracting Miller Capacitance, C_M

1.6 Miller Capacitance, C_M

Using $G_{v(Max)}$ found in the previous section, the Miller Capacitance C_M was found analyzing the equivalent circuit in Figure 2.

$$Z_C = \frac{1}{\omega C} \implies C = \frac{1}{\omega Z_C}$$

$$\text{Where } \omega = (2\pi \cdot 7.04 \text{ MHz}) \approx 44.2 \left[M \frac{\text{rad}}{\text{s}} \right]$$

$$V_R = V_0 \left(\frac{560\Omega}{(560\Omega + Z_C)} \right) \text{ (Voltage divider rule)}$$

$$\text{Since } V_0 = 1V ; V_R = 400mV$$

$$Z_C = 560\Omega \left(\frac{V_0}{V_R} - 1 \right) \implies 560\Omega \left(\frac{1}{400 \cdot 10^{-3}} - 1 \right)$$

$$Z_C = 840\Omega$$

$$\text{Since } C = \frac{1}{(\omega Z_C)} \implies \frac{1}{(44.2 \cdot 10^6) \cdot 840} = 26.9pF$$

$$C_M = \frac{C}{|G_{v(Max)}| + 1} \implies \frac{26.9pF}{8.9dB}$$

$$\therefore C_M = \boxed{3.02pF}$$

(Note: At the end of this step, the other end of R_{11} was soldered).

2 Buffer Amplifier

Figure 3 shows the schematic of the Buffer amplifier.

Such a circuit is a source-follower, and therefore has no impedance gain and a high input impedance. The function generator was connected to C_{37} with the $1.5k\Omega$ resistor. The frequency used was $7.04V$ and the amplitude was $1V_{pp}$.

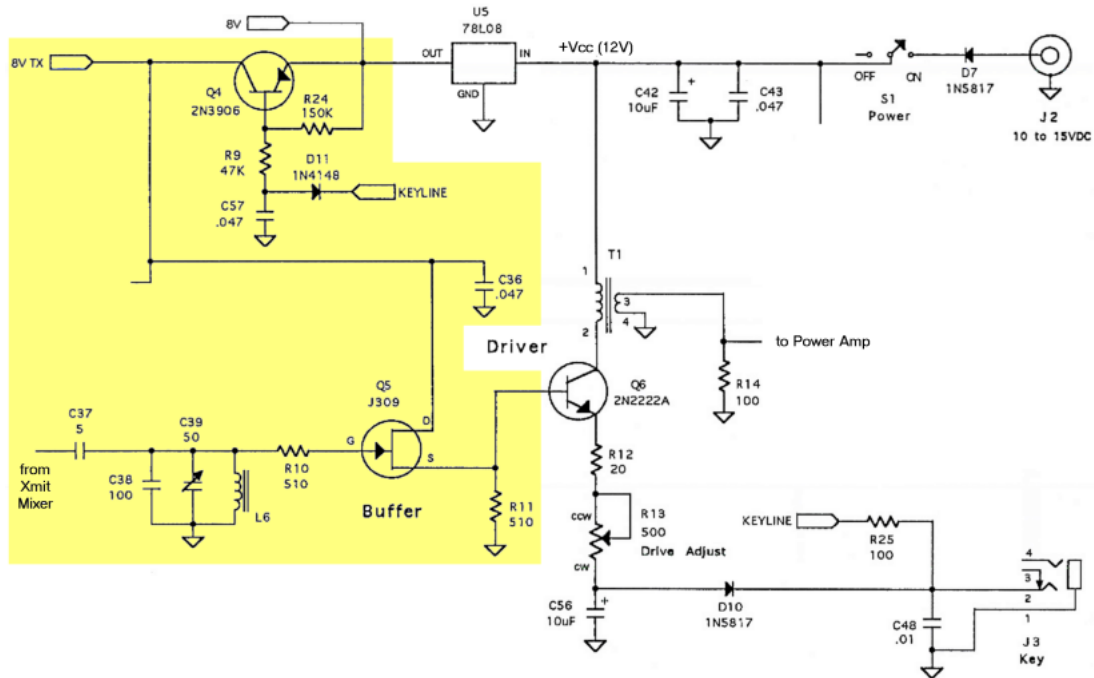


Figure 3: Circuit Schematic for the Buffer Amplifier

2.1 Max Voltage Across R_{10}

C_{39} was adjusted for maximum voltage. The measured maximum value was $65.1V_{RMS}$.

2.2 Voltage Gain G_v across R_{11}

The voltage gain across R_{11} was calculated to be:

$$G_v = 20 \log \left(\frac{v}{v_i} \right) \Rightarrow 20 \log \left(\frac{1.09V}{65.1mV} \right) = \boxed{24.5dB}$$

2.3 Power Gain, G_P

Given that a $1.5k\Omega$ resistor is at the input and a 510Ω is at the load, the power gain was calculated to be:

$$G_P = 10 \log \left(\frac{P}{P_0} \right) \Rightarrow 10 \log \left(\frac{2.33 \text{ mW}}{2.83 \mu \text{ W}} \right) = \boxed{29.2 \text{ dB}}$$